

COL215 HW Assignment 2 - 4-Digit 7-Segment Display

Submission By :

Yash Rawat
2023CS50334

Priyanshi Gupta
2023CS10106

Department of Computer Science and Engineering
Indian Institute of Technology, Delhi

September 01, 2024

 
 


Figure 18. Common anode circuit node.

1 Assignment Problem Statement

Design a combinational circuit that takes a single 4-bit hexadecimal or decimal digit input from the switches and produces a 7-bit output for the seven-segment display of Basys 3 FPGA board. Extend the design to create a circuit that drives all 4 displays for displaying 4 digits together.

1.1 Overview of Assignment :

The assignment requires us to design three modules with the following inheritance logic :

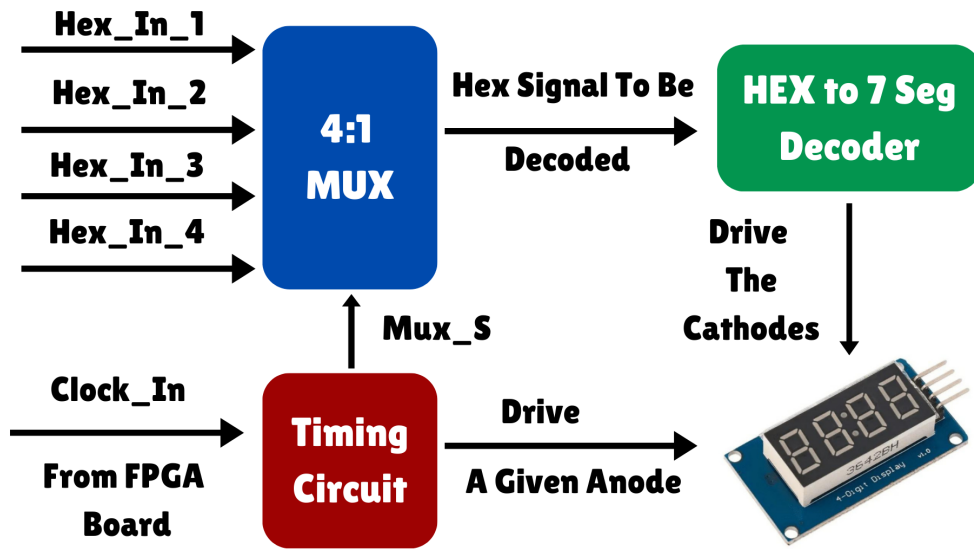


Figure 1: Overview of Design of Assignment

We will also define a wrapper VHD File - 7Seg_Display to implement all of the logic and take respective inputs for all the components. The 4:1 MUX accepts the 4 Hexadecimal input signals to be displayed on 7 Segment Display. The timing circuit governs the anode to be displayed as well as provides the corresponding selection bits to MUX. Finally the decoder module decodes the 7-bits using minimised combinational logic to drive the cathodes of display. The in-depth explanation of all the three components and their inheritance is explained later.

2 Design Decisions of Overall Project

2.1 Hexadecimal Digits

Since we are implementing display of 4 hexadecimal digits, we require 16 input bits from the board (accepted from the 16 switches available on board) to represent the input's to . We use the following symbols for representation on 7 Segment display :



Figure 2: Caption

2.2 Truth Table - For BCD to 7 Segment Display

Digits & Input Bits					7 Segment Display							Min-Terms: $f(A, B, C, D)$
Digit	A	B	C	D	a	b	c	d	e	f	g	Min-Term Index
0	0	0	0	0	1	1	1	1	1	1	0	m_0
1	0	0	0	1	0	1	1	0	0	0	0	m_1
2	0	0	1	0	1	1	0	1	1	0	1	m_2
3	0	0	1	1	1	1	1	1	0	0	1	m_3
4	0	1	0	0	0	1	1	0	0	1	1	m_4
5	0	1	0	1	1	0	1	1	0	1	1	m_5
6	0	1	1	0	1	0	1	1	1	1	1	m_6
7	0	1	1	1	1	1	1	0	0	0	0	m_7
8	1	0	0	0	1	1	1	1	1	1	1	m_8
9	1	0	0	1	1	1	1	0	0	1	1	m_9
A	1	0	1	0	1	1	1	0	1	1	1	m_{10}
b	1	0	1	1	0	0	1	1	1	1	1	m_{11}
C	1	1	0	0	1	0	0	1	1	1	0	m_{12}
d	1	1	0	1	0	1	1	1	1	0	1	m_{13}
E	1	1	1	0	1	0	0	1	1	1	1	m_{14}
F	1	1	1	1	1	0	0	0	1	1	1	m_{15}

2.3 Minimizing the Combinational Logic using K-Maps

2.3.1 Segment a

$$f(A, B, C, D)$$

		C, D			
		00	01	11	10
A, B	00	1	0	1	1
	01	0	1	1	1
	11	1	0	1	1
	10	1	1	0	1

The reduced formula for segment a using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = A'B'D' + A'BD + AC'D' + AB'C' + A'C + BC + CD'$$

2.3.2 Segment b

$$f(A, B, C, D)$$

		C, D			
		00	01	11	10
A, B	00	1	1	1	1
	01	1	0	1	0
	11	0	1	0	0
	10	1	1	0	1

The reduced formula for segment b using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = A'C'D' + A'CD + AC'D + B'D' + A'B'$$

2.3.3 Segment c

$$f(A, B, C, D)$$

		C, D			
		00	01	11	10
A, B	00	1	1	1	0
	01	1	1	1	1
	11	0	1	0	0
	10	1	1	1	1

The reduced formula for segment c using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = A'CD + A'C' + A'B + C'D + AB'$$

2.3.4 Segment d

$f(A, B, C, D)$

		C, D			
		00	01	11	10
A, B	00	1	0	1	1
	01	0	1	0	1
	11	1	1	0	1
	10	1	0	1	0

The reduced formula for segment d using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = A'B'D' + B'CD + BC'D + BCD' + A'C'D'$$

2.3.5 Segment e

$f(A, B, C, D)$

		C, D			
		00	01	11	10
A, B	00	1	0	0	1
	01	0	0	0	1
	11	1	1	1	1
	10	1	0	1	1

The reduced formula for segment e using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = B'C'D' + AB + CD' + AC$$

2.3.6 Segment f

$f(A, B, C, D)$

		C, D			
		00	01	11	10
A, B	00	1	0	0	0
	01	1	1	0	1
	11	1	0	1	1
	10	1	1	1	1

The reduced formula for segment f using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = A'BC' + BCD' + AB' + AC + C'D'$$

2.3.7 Segment g

$f(A, B, C, D)$

		C, D			
		00	01	11	10
A, B	00	0	0	1	1
	01	1	1	0	1
	11	0	1	1	1
	10	1	1	1	1

The reduced formula for segment g using the mentioned K-Map reduction is as following :

$$f(A, B, C, D) = A'B'C + A'BC'$$

$$CD' + AB' + AD$$

3 Design Decisions for Modules

3.1 Hexadecimal-To-7-Segment-Display

Decoder is a combinational module which accepts the 4 input bits from the **MUX_4BIT** to be displayed on a seven segment display. Then the decoder implements the reduced combinational logic and sets the respective states of cathodes to drive the output on the seven segment display.

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity seven_seg_decoder_hex is
5     port (
6         dec_in : in std_logic_vector(3 downto 0);
7         dec_out : out std_logic_vector(6 downto 0)
8     );
9 end seven_seg_decoder_hex;
10
11 architecture Behavioral of seven_seg_decoder_hex is
12     signal A, B, C, D : std_logic;
13
14     -- Basys 3 board uses Active Low Pins hence the values are inverted
15     -- Logic from actual reduced expression using K-map
16     -- (Sum of Min terms method)
17 begin
18     Seg_Decoder_HEX : process(dec_in)
19     begin
20         D <= dec_in(0);
21         C <= dec_in(1);
22         B <= dec_in(2);
23         A <= dec_in(3);
24         dec_out(0) <= -- Logic of a
25         dec_out(1) <= -- Logic of b
26         dec_out(2) <= -- Logic of c
27         dec_out(3) <= -- Logic of d

```

```

28         dec_out(4) <= -- Logic of e
29         dec_out(5) <= -- Logic of f
30         dec_out(6) <= -- Logic of g
31
32     end process;
33 end Behavioral;

```

Listing 1: Decoder Code

3.2 4:1 MUX

The board is used to generate 4 hexadecimal inputs, one for each seven segment display. Since the cathodes of all the 4 displays are common, the timer circuit provides select bits : *dec_in* which also corresponds to the anode, i.e. one of the four 7 Segment displays which are being driven. The implemented MUX_Process chooses the hexadecimal input to be displayed using case statement, which is passed onto the decoder module to be decoded into 7 segment bits.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity MUX_4BIT is
5      port(
6          mux_s : in std_logic_vector(1 downto 0);
7          mux_d0 : in std_logic_vector(3 downto 0);
8          mux_d1 : in std_logic_vector(3 downto 0);
9          mux_d2 : in std_logic_vector(3 downto 0);
10         mux_d3 : in std_logic_vector(3 downto 0);
11         mux_out_to : out std_logic_vector(3 downto 0)
12     );
13 end MUX_4BIT;
14 architecture Behavioral of MUX_4BIT is
15 begin
16     MUX_Process: process(mux_s, mux_d0, mux_d1, mux_d2, mux_d3)
17     begin
18         case mux_s is
19             when "00" =>
20                 mux_out_to <= mux_d0;
21             when "01" =>
22                 mux_out_to <= mux_d1;
23             when "10" =>
24                 mux_out_to <= mux_d2;
25             when "11" =>
26                 mux_out_to <= mux_d3;
27             when others =>
28                 mux_out_to <= "0000";
29         end case;
30     end process;
31 end Behavioral;


```

Listing 2: 4:1 MUX

 3.3 Timing Circuit

Timing circuit is the Crux of this project. Since the cathodes of all the four 7 Segment displays are common, we need a way to cycle through the different anodes and a way to keep track which hexadecimal input is to be displayed on the given anode (which is what the 4:1 MUX module implements).

This module also accepts **clk_in** from the Basys3 board, an inbuilt 100 MHz clock. For our practical purposes using such a high frequency clock is not viable since it may cause flickering issues, care is taken to implement a **new_clk** which uses a **counter** and **N** to increase the time period from 10 *ns* to 10.24 *ms*, a frequency 97.65625 *Hz* as given below.



Since human eye's vision is persistent at these refresh rates, the **MUX_PROC** process changes the state of **mux_select_counter** cyclically according to the **rising_edge** of **new_clk** and assigns it to **mux_select** which goes to MUX module. This part handles the cyclical change of anodes which allow us to display all 4 digits perceived at once.

Finally the **ANODE_select** process chooses the anode states for choosing which anode the digit is to be displayed upon.

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6 entity Timing_block is
7     Port (
8         clk_in : in STD_LOGIC; -- 100 MHz input clock
9         reset : in STD_LOGIC; -- Reset signal (Resetting the
10             internal signals to known states)
11         mux_select : out STD_LOGIC_VECTOR (1 downto 0); -- Signal
12             for the mux
13         anodes_tout : out STD_LOGIC_VECTOR (3 downto 0) -- Anodes
14             signal for display
15     );
16 end Timing_block;
17
18 architecture Behavioral of Timing_block is
```



```

16     constant N : integer := 511; -- <need to select correct value>
17     signal counter: integer := 0;
18     signal mux_select_counter : STD_LOGIC_VECTOR (1 downto 0) := "00
";
19     signal new_clk : STD_LOGIC := '0';
20
21 begin
22 --Process 1 for dividing the clock from 100 Mhz to 1Khz - 60hz
23 -- Gives rise to a clock with t = 10.24 ms or f = 97.65625 Hz
24     CLK_PROC: process(clk_in, reset)
25     begin
26         if(reset = '1') then
27             counter <= 0;
28             new_clk <= '0';
29         elsif rising_edge(clk_in) then
30             if counter = N then
31                 counter <= 0;
32                 new_clk <= not new_clk;
33             else
34                 counter <= counter + 1;
35             end if;
36         end if;
37     end process;
38
39 --Process 2 for mux select signal
40     MUX_PROC: process(new_clk, reset)
41     begin
42         if(reset = '1') then
43             mux_select_counter <= "00";
44         elsif(rising_edge(new_clk)) then
45             mux_select_counter <= mux_select_counter + 1;
46         end if;
47         mux_select <= mux_select_counter;
48     end process;
49 --Process 3 for anode signal
50     ANODE_select: process(mux_select_counter, reset)
51     begin
52         if(reset = '1') then
53             anodes_tout <= "1111";
54         elsif(mux_select_counter = "00") then
55             anodes_tout <= "1110";
56         elsif (mux_select_counter = "01") then
57             anodes_tout <= "1101";
58         elsif (mux_select_counter = "10") then
59             anodes_tout <= "1011";
60         elsif (mux_select_counter = "11") then
61             anodes_tout <= "0111";
62         end if;
63     end process;
64
65 end Behavioral;

```

Listing 3: Timing Circuit

Note that whenever the board detects reset, the **counter** and the **new_clk** is restored to a known default. Also all the displays/anodes are switched off to show the circuit is in a reset state.

3.4 7Seg_Display - The Final Wrapper

This instantiates all the other modules as entities and implements the necessary signals for input from the board to the modules and the output back to board.

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity display_seven_seg is
5     Port (
6         clock_in : in STD_LOGIC; -- For Timing_Block
7         reset_timer : in STD_LOGIC; -- For Timing_Block
8         d0: in std_logic_vector(3 downto 0); -- For MUX_Block
9         d1: in std_logic_vector(3 downto 0); -- For MUX_Block
10        d2: in std_logic_vector(3 downto 0); -- For MUX_Block
11        d3: in std_logic_vector(3 downto 0); -- For MUX_Block
12        an : out STD_LOGIC_VECTOR (1 downto 0); -- For Timing_Block
13        seg : out STD_LOGIC_VECTOR (3 downto 0) -- For Timing_Block
14    );
15 end display_seven_seg;
16
17 architecture Behavioral of display_seven_seg is
18
19     component Timing_block is
20         Port (
21             clk_in : in STD_LOGIC; -- 100 MHz input clock
22             reset : in STD_LOGIC; -- Reset Signal
23             mux_select : out STD_LOGIC_VECTOR (1 downto 0); -- IN to
24             MUX_Block
25             anodes_tout : out STD_LOGIC_VECTOR (3 downto 0) --
26             Anodes signal for display
27         );
28     end component;
29
30     component seven_seg_decoder_hex is
31         port (
32             dec_in : in std_logic_vector(3 downto 0);
33             dec_out : out std_logic_vector(6 downto 0)
34         );
35     end component;
36
37     component MUX_4BIT is
38         port(
39             mux_s : in std_logic_vector(1 downto 0);
40             mux_d0 : in std_logic_vector(3 downto 0);
41             mux_d1 : in std_logic_vector(3 downto 0);
42             mux_d2 : in std_logic_vector(3 downto 0);
43             mux_d3 : in std_logic_vector(3 downto 0);

```

```

42         mux_out_to : out std_logic_vector(3 downto 0)
43     );
44 end component;
45
46 signal mux_sel: std_logic_vector(1 downto 0);
47 signal mux_out_dec: std_logic_vector(3 downto 0);
48
49 begin
50     Timer_Block : -- UUT and Port Mapping for Timing Circuit
51
52     MUX_Block :-- UUT and Port Mapping for MUX
53
54     Decoder_Block : -- UUT and Port Mapping for Decoder
55
56 end Behavioral;

```

4 Submission Details

4.1 Simulation Snapshots

4.1.1 Simulation of Hexadecimal Decoder

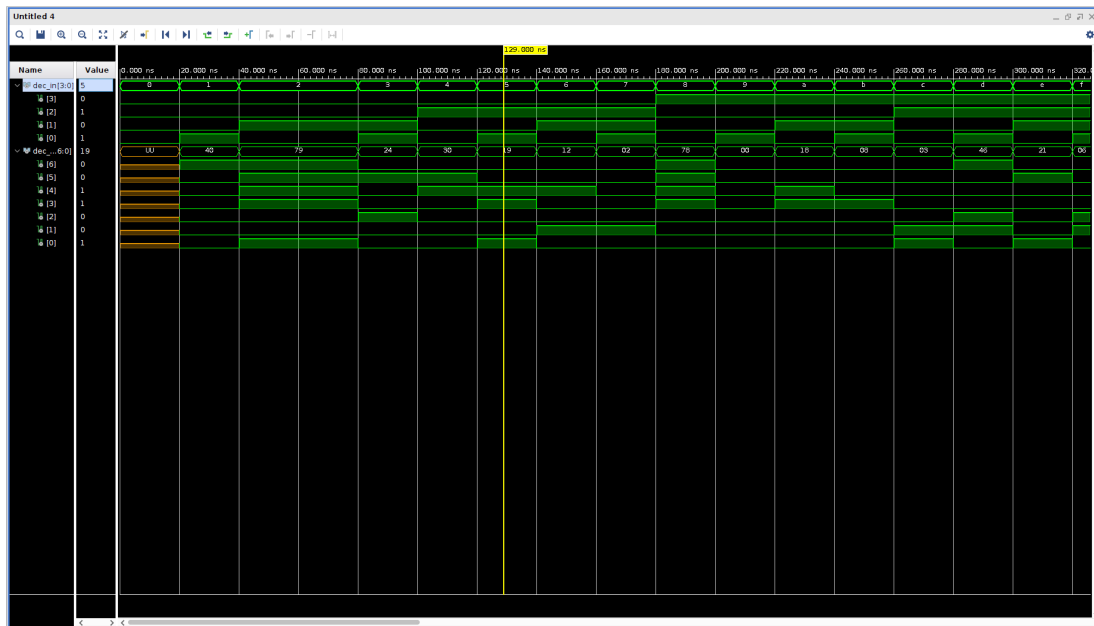


Figure 3: Simulation of Decoder

A point to note is that the output seems flipped in comparison to Truth Table. This is because the cathode pins on the Basys board work in low configuration. This holds everywhere in the simulation and the implementation.

4.1.2 Simulation of 4:1 MUX

4.1.3 Simulation of Timing Circuit

4.2 Schematic Snapshots

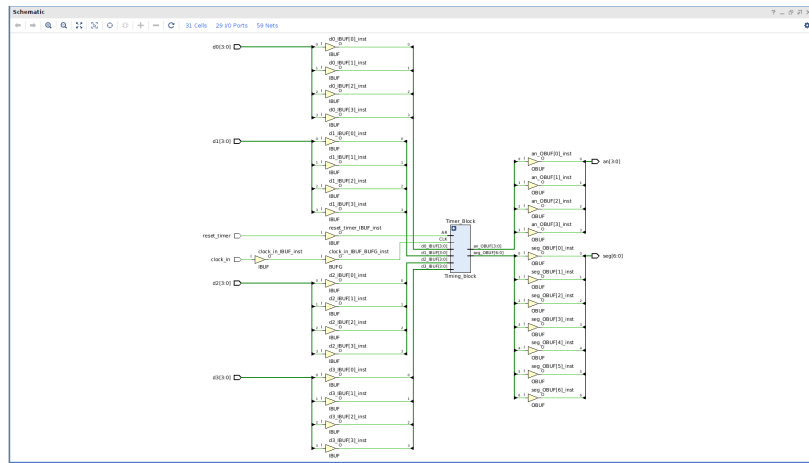


Figure 4: Schematic

4.3 Resource Utilization

```
1. Slice Logic
-----
```

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	52	0	0	20800	0.25
LUT as Logic	52	0	0	20800	0.25
LUT as Memory	0	0	0	9600	0.00
Slice Registers	35	0	0	41600	0.08
Register as Flip Flop	35	0	0	41600	0.08
Register as Latch	0	0	0	41600	0.00
F7 Muxes	0	0	0	16300	0.00
F8 Muxes	0	0	0	8150	0.00

* Warning! The Final LUT count, after physical optimizations and full implementation, is typically lower. Run opt_design after synthesis, if not already completed.

```
2. Memory
-----
```

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	50	0.00
RAMB36/FIFO*	0	0	0	50	0.00
RAMB18	0	0	0	100	0.00

* Note: Each Block RAM Tile only has one FIFO logic available and therefore can accommodate only one FIFO36E1 or one FIFO18E1. However, if a FIFO18E1 occupies a B

```
3. DSP
-----
```

Site Type	Used	Fixed	Prohibited	Available	Util%
DSPs	0	0	0	90	0.00

Figure 5: Resource Utilization

4.4 Output on FPGA Board

 


Figure 6: Basys Board output 1

 


Figure 7: Basys Board output 2